

- [124] One of the technical limitations of capacitive proximity sensors is the fact that they
- Are not very sensitive to objects that are poor electrical conductors.
 - Are insensitive to objects that reflect light.
 - Are insensitive to metallic objects.
 - Cannot be used with oscillators
 - Require extreme voltages in order to function properly
- [125] The power factor in an ac circuit is defined as
- The actual power divided by the maximum power the circuit can handle.
 - The ratio of the real power to the imaginary power.
 - The ratio of the apparent power to the true power.
 - The ratio of the true power to the apparent power.
 - The ratio of the imaginary power to the apparent power.
- [126] The amount of current that a silicon photodiode can deliver in direct sunlight depends on
- The forward breakover voltage.
 - The thickness of the substrate.
 - The surface area of the P-N junction.
 - The applied voltage.
 - The reverse bias.
- [127] In an amplifier that employs a P-Channel JFET, the device can usually be replaced with an N-channel JFET having similar specifications, provided that
- All the resistors are reversed in polarity for the circuit in question
 - The power supply polarity is reversed for the circuit in question
 - The drain, rather than the source, is placed at signal ground
 - The output is taken from the source, rather than from the drain.
- [128] Secondary breakdown occurs in
- MOSFET but not in BJT
 - Both MOSFET and BJT
 - BJT but not in MOSFET
 - None of these
- [129] In a transistor
- $\beta = \alpha / (\alpha + 1)$
 - $\beta = \alpha / (1 - \alpha)$
 - $\alpha = \beta / (\beta - 1)$
 - $\alpha = (\beta + 1) / \beta$
- [130] In a multi-stage RC coupled amplifier the coupling capacitor _____
- Limits the low frequency response
 - Limits the high frequency response
 - Does not affect the frequency response
 - Block the DC component without affecting the frequency response

DIGITAL ELECTRONICS

- [1] It is required to construct a counter to count upto 100(decimal). The minimum number of flipflops required to construct the counter is
- 8
 - 7
 - 6
 - 5
- [2] The gate that assumes the 1 state, if and only if the input does not take a 1 state is called **D**.....
- AND gate
 - NOT gate
 - NOR gate
 - Both b and c

[3] For NOR circuit SR flip flop the not allowed condition is....

- A. $S=0, R=0$
- B. $S=0, R=1$
- C. $S=1, R=1$**
- D. $S=1, R=0$

HINT: - When $S=R=1$ the output is subject to unpredictable behaviour when S and R return to 0 simultaneously.

[4] A bistable multivibrator is a

- A. Free running oscillator
- B. Triggered oscillator**
- C. Saw tooth wave generator
- D. Crystal oscillator

[5] For a large values of $|V_{DS}|$, a FET behave as

- A. Voltage controlled resistor
- B. Current controlled current source
- C. Voltage controlled current source**
- D. Current controlled resistor

[6] When a step input is given to an op-amp integrator, the output will be

- A. a ramp**
- B. a sinusoidal wave
- C. a rectangular wave
- D. a triangular wave with dc bias

[7] In a full-wave rectifier without filter, the ripple factor is

- A. 0.482**
- B. 1.21
- C. 1.79
- D. 2.05

[8] Hysteresis is desirable in Schmitt-trigger, because

- A. Energy is to be stored/discharged in parasitic capacitance
- B. Effects of temperature would be compensated
- C. Devices in the circuit should be allowed time for saturation and desaturation**
- D. It would prevent noise from causing false triggering

[9] For a 10-bit DAC, the Resolution is defined by which of the following

- a) 1024
- b) $1/1024$**
- c) 10
- d) None

[10] SRAM full form is

- a) Serial Read Access Memory
- b) Static Random Access Memory**
- c) Static Read-only Access memory

[11] What are the minimum number of 2 to 1 multiplexers required to generate a 2 input AND gate and a 2 input Ex-OR gate?

- A) 1 and 2**
- B) 1 and 3
- C) 1 and 1
- D) 2 and 2

[12] The output of a logic gate is '1' when all its inputs are at logic '0'. Then gate is either

- A) A NAND or an EX-OR gate
- B) A NOR or an EX-NOR gate**
- C) An OR or a EX-NOR gate
- D) An AND or an Ex-OR gate

[13] A PLA can be used

- A) As a microprocessor
- B) As a dynamic memory
- C) To realise a sequential logic
- D) To realise a combinational logic**

[14] A dynamic RAM consists of

- A) 6 Transistors
- B) 2 Transistors and 2 Capacitors
- C) 1 Transistor and 1 Capacitor**
- D) 2 Capacitor only

[15] When a CPU is interrupted, it

- A) Stops execution of instructions
- B) Acknowledges interrupt and branches of subroutine**
- C) Acknowledges interrupt and continues
- D) Acknowledges interrupt and waits for the next instruction from the interrupting device.